

23-24

MAULANA ABUL KALAM AZAD UNIVERSITY OF TECHNOLOGY, WEST BENGAL



Paper Code : BCAC101 Digital Electronics
UPID : 100

downloaded from GradGuru99.com

Full Marks : 70

Time Allotted : 3 Hours

The Figures in the margin indicate full marks.

Candidate are required to give their answers in their own words as far as practicable

Group-A (Very Short Answer Type Question)

[1 x 10 = 10]

1. Answer any ten of the following :

- (i) Dual of NAND function is _____
- (ii) The half adder has _____ inputs and full adder has _____ inputs.
- (iii) What is the indication of a short to ground in the output of a driving gate?
- (iv) How is a J-K flip-flop made to toggle?
- (v) Ripple counters are also called _____
- (vi) Convert 128 to binary
- (vii) The NAND gate can function as a NOT-gate if _____
- (viii) Reduce the expression $f = A[B + C'(AB + AC)']$
- (ix) What is the minimum number of two-input NAND gates used to perform the function of two input OR gate?
- (x) _____ are the universal gates.
- (xi) Full subtractor is used to perform subtraction of _____ bits.
- (xii) How many data select lines are required for selecting eight inputs?

GRADGURU99.COM

Group-B (Short Answer Type Question)

Answer any three of the following :

[5 x 3 = 15]

- 1. Represent a NAND gate as OR gate using De Morgan's law and explain. [5]
- 2. What is the difference between a half adder and a full adder? [5]
- 3. Explain the difference between decoder & demultiplexer [5]
- 4. What is toggling state & race condition? [5]
- 5. Explain the difference between PISO & PIPO. [5]

visit GradGuru99.com

Group-C (Long Answer Type Question)

Answer any three of the following :

[15 x 3 = 45]

- 1. (a) Explain the difference between sequential circuit & combinational circuit. [7]
- (b) Explain SR Flip-flop in detail. What is the disadvantage of it and how it can be eliminated? [8]
- 2. (a) Design a combination circuits for a half & full subtractor and explain it in detail. [10]
- (b) Explain the limitations of half subtractor over full subtractor. [5]
- 3. (a) Design a full adder using 3:8 decoder. [8]
- (b) Explain the difference between multiplexer & demultiplexer [7]
- 10. (a) With logic diagram and truth table explain the working JK Flip-flop. Also obtain its characteristic equation. [7]
- (b) How JK flip-flop is the refinement of RS flip-flop? [4]
- (c) Explain D- Flip-flop in detail. [4]
- 11. (a) What is multiplexer? Explain 4X1 multiplexer. [2+7]
- (b) Explain encoder with proper diagram, truth table, Boolean expression [6]

GradGuru99.com

*** END OF PAPER ***